

# Electrotechnology Lab Report

**Name:** Sharon Olorunniwo

**Student Number:** 16323766

**Partners:** Thuraya A. Shaheen  
Edvinas Teišerskis

**Performed:** Lab Session 2  
18th November 2016  
4p.m. - 6p.m.

**Date:** 22nd November 2016


**Class:** Electrotechnology CS1025

## **INTRODUCTION**


This experiment uses the concept of elementary direct current to help demonstrate and verify Ohm's Law and Kirchoff's Current and Voltage Laws .

# Apparatus


Resistors

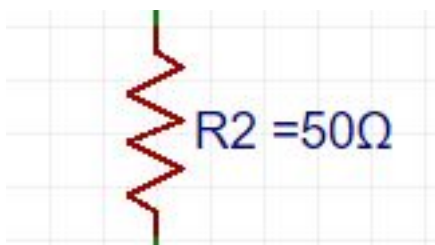

D.C Power Supply (5V)

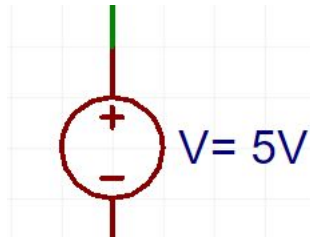


LED (Light emitting diode)

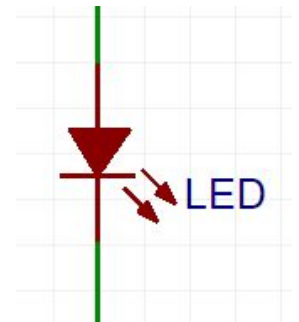

MultiMeter



BreadBoard

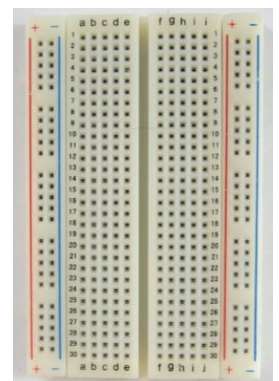

## **Background**

### **OHM'S LAW**

One of the key components of this experiment was the resistor. A resistor is a two-terminal element which impedes the flow of electrical current. It converts some of the electrical energy into another form of energy. The degree of impedance is measured in **ohm's  $\Omega$** . Every material has resistance to a certain extent. **Resistors are also referred to as Ohmic Materials**. A material is deemed ohmic when there is a linear relationship between the applied voltage and the current. **Ohm's Law states that the current through a conductor between two points is directly proportional to the voltage across the two points.**

$$v(t) = Ri(t)$$

- 'R' is known as the Resistance
- 't' is time
- 'v(t)' is voltage across the terminals
- 'i(t)' is the current flowing through the device

To find the Voltage, ( V )

$$[ V = I \times R ] \quad V (\text{volts}) = I (\text{amps}) \times R (\Omega)$$

To find the Current, ( I )


$$[ I = V \div R ] \quad I (\text{amps}) = V (\text{volts}) \div R (\Omega)$$

To find the Resistance, ( R )

$$[ R = V \div I ] \quad R (\Omega) = V (\text{volts}) \div I (\text{amps})$$
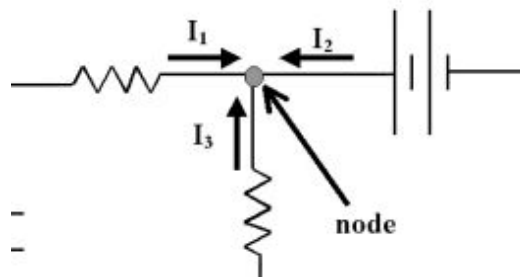
## Kirchoffs Current Law

**Kirchoff's Current Law states that the: “total current or charge entering a junction or node is exactly equal to the charge leaving the node as it has no other place to go except to leave, as no charge is lost within the node”.** A principal node is a branch point where the currents divide or combine. Current entering the node is given a positive sign and that leaving is given a negative sign, in other words the sum of all the currents entering and leaving a node must be equal to zero.




$$I_1 = I_2 + I_3$$

$$I_1 + (-I_2) + (-I_3) = 0$$

$$\sum I_{Node} = 0$$


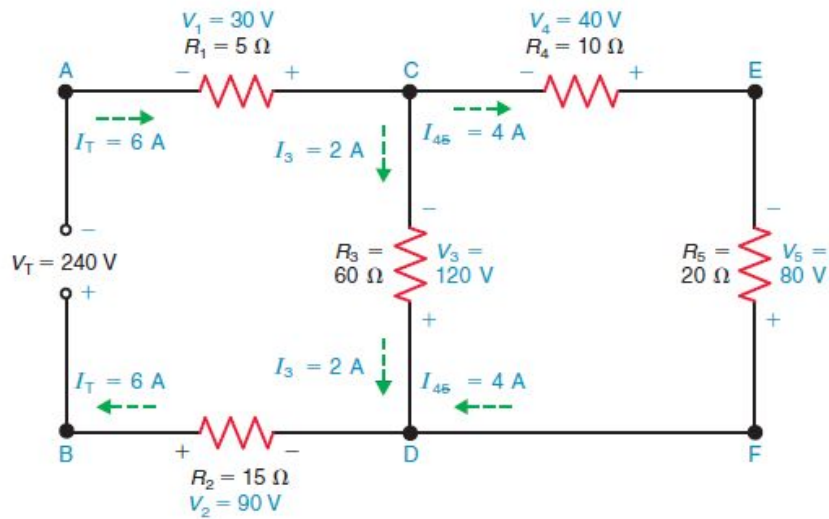
$$I(\text{exiting}) + I(\text{entering}) = 0.$$



## Kirchoff's Voltage Law

**Kirchhoff's Voltage Law states that: "in any closed loop network, the total voltage around the loop is equal to the sum of all the voltage drops within the same loop"** In other words the sum of all voltages within the loop must be equal to zero. The electrons flowing into the receiving end of the resistor causes that end to be negative in respect to the other. For a normal voltage source electrons flow from negative to positive. This idea by Kirchoff is known as the **Conservation of Energy**.

$$\sum v_{rise} = \sum v_{drop}$$

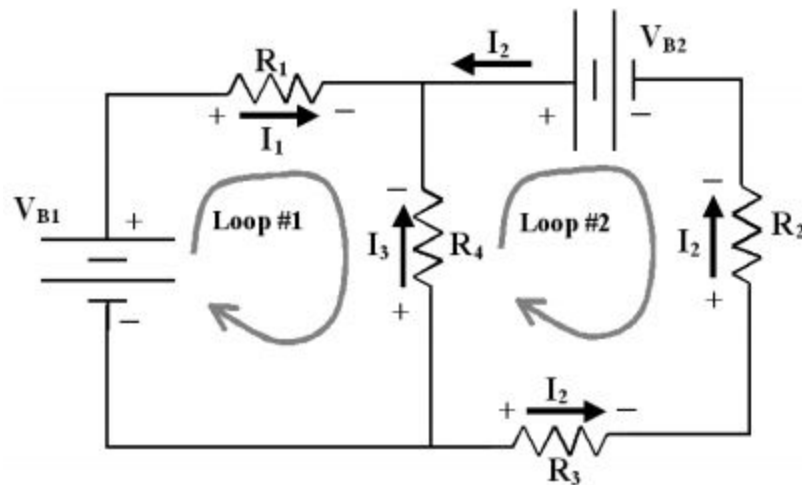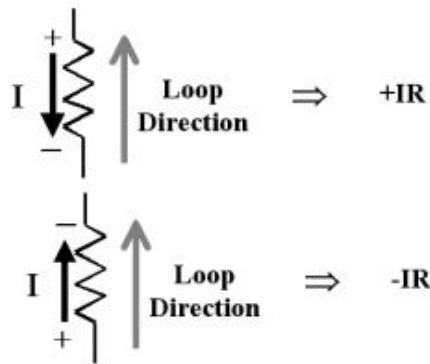


## **METHOD**

Before we started the experiment we measured the resistance of each of the resistors with the multimeter to ensure we were using the right ones. We did this by setting the scale on the multimeter. We then used the multimeter to measure the voltage of the d.c. power source.
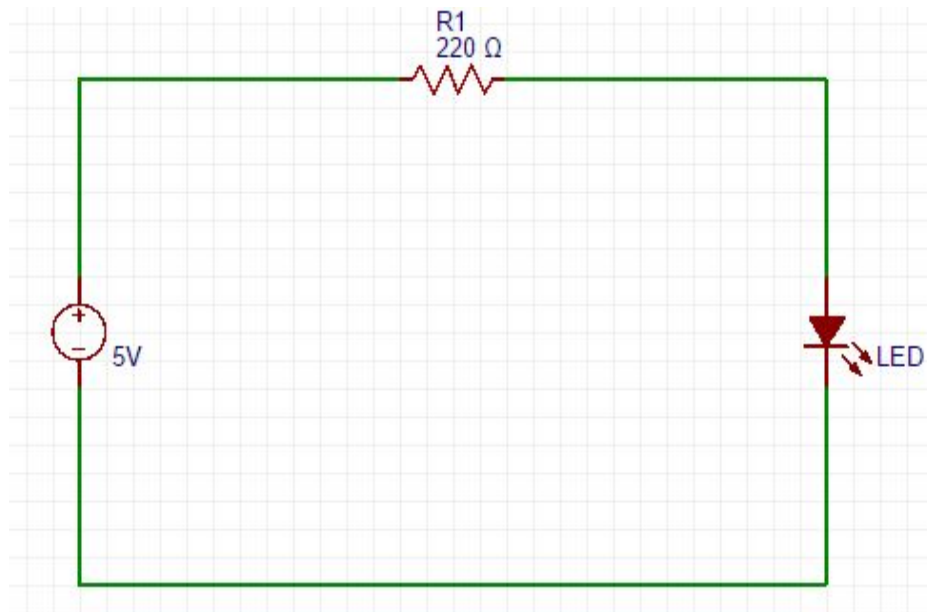
## **Circuit One**

This consists of a  $220\ \Omega$  resistor connected to a 5V D.C power source and an LED (Light Emitting Diode).



## **Method**

1. Set up the circuit shown in the diagram above using D.C. power source, 220 resistor and the LED
2. Measure the current through the resistor using a multimeter. Put the results on the table.
3. Measure the voltage drop of the resistor in the circuit using the multimeter. Put the results on the table
4. Measure the current through the LED using a multimeter. Put the results on the table.

## DATA

COMPONENT	RESISTOR	LED
Resistance ( $\Omega$ )	480	0.004
Voltage (V)	2.25	4.8
Current (mA)	10	10

## RESULTS / CALCULATIONS


The LED lights up. This shows that the circuit is closed and working correctly.

$$\begin{aligned}\text{Resistance of LED} &= V / I \\ &= 10 \times 10^{-3} \text{ V} / 2.25 \text{ mA} \\ &= 0.004 \Omega\end{aligned}$$


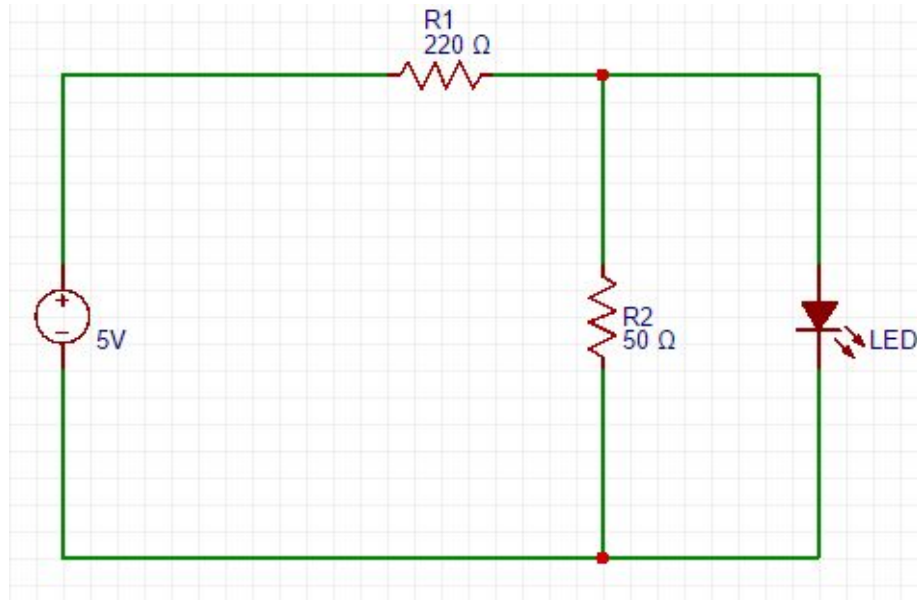
## Circuit Two

This circuit was made by adding a  $50\ \Omega$  resistor in parallel to the original circuit



## Method

Repeat the steps above for this circuit.

## DATA

COMPONENT	BASE RESISTOR	SECOND RESISTOR	LED
Resistance ( $\Omega$ )	220	50	0
Voltage (V)	5.6	1.3	
Current (mA)	26	25	0


## RESULTS / CALCULATIONS

The LED has a very dim glow.

$$\begin{aligned}\text{Resistance of the LED} &= V / I \\ &= 0 \text{ V} / 1.3 \text{ mA} \\ &= 0 \, \Omega\end{aligned}$$
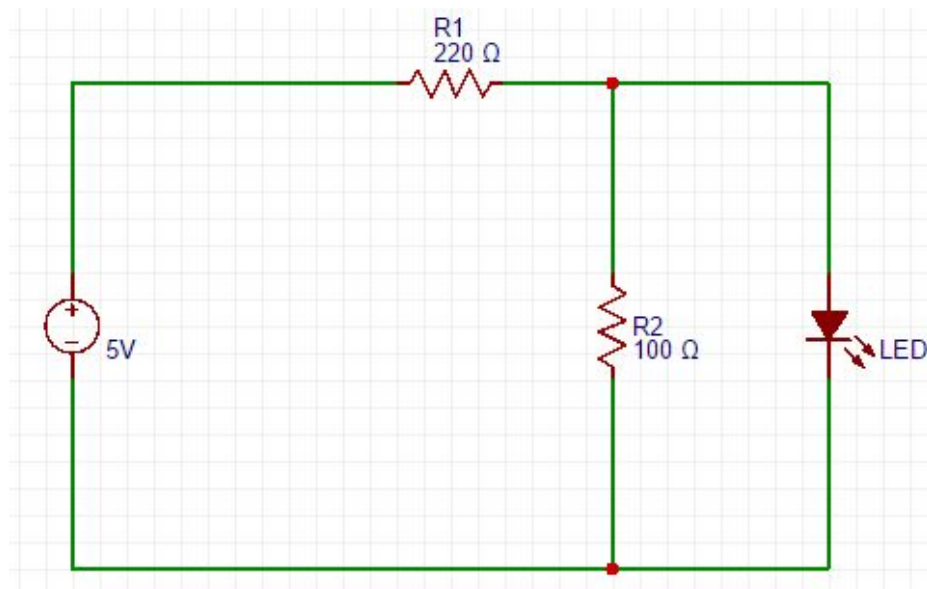
## Circuit Three

This circuit was made by replacing the  $50 \, \Omega$  resistor with a  $100 \, \Omega$  resistor



## Method

Repeat the steps above for this circuit.

## DATA

COMPONENT	BASE RESISTOR	SECOND RESISTOR	LED
Resistance ( $\Omega$ )	220	100	0.00048
Voltage (V)	4.8	2.05	
Current (mA)	22	21	1


## RESULTS / CALCULATIONS

The LED is slightly brighter than the case with the 50  $\Omega$

$$\begin{aligned}\text{Resistance of the LED} &= V / I \\ &= 1 \times 10^{-3} \text{ V} / 2.05 \text{ mA} \\ &= 0.000488 \Omega\end{aligned}$$
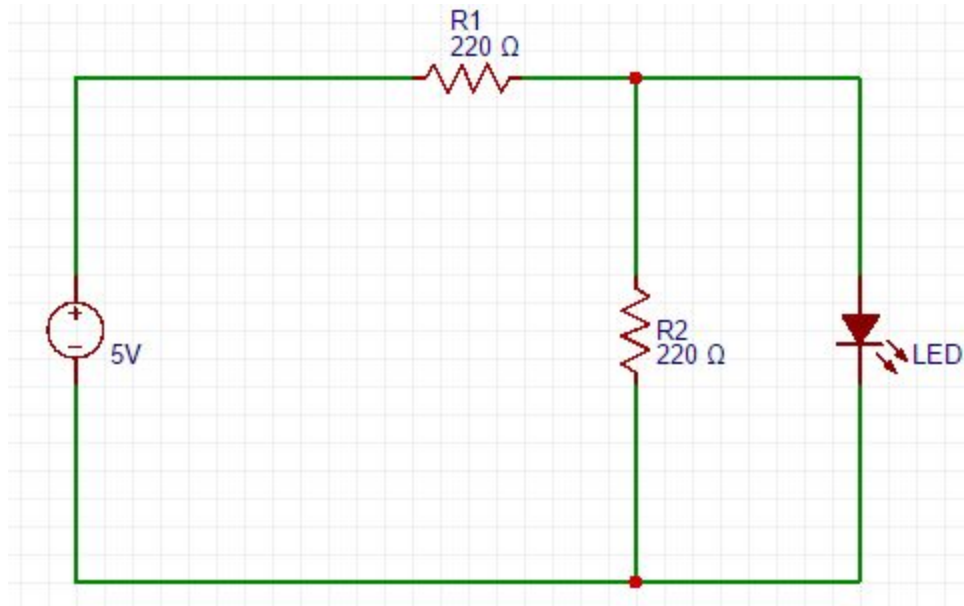
## Circuit Four

This circuit was made by replacing the  $100\ \Omega$  resistor with a  $220\ \Omega$  resistor



## Method

Repeat the steps above for this circuit.

## DATA

COMPONENT	BASE RESISTOR	SECOND RESISTOR	LED
Resistance ( $\Omega$ )	220	220	$1.5 \times 10^{-3}$
Voltage (V)	3.9	3	
Current (mA)	18	13.5	4.5

## **RESULTS / CALCULATIONS**

The LED is slightly brighter than the case with the 100  $\Omega$

$$\begin{aligned}\text{Resistance of the LED} &= V / I \\ &= 4.5 \times 10^{-3} \text{ V} / 3 \text{ mA} \\ &= 1.5 \times 10^{-3} \Omega\end{aligned}$$

## **CONCLUSION/OBSERVATIONS**

In all cases the voltage was around 7V, this proves Kirchhoff's Voltage Law.

### **Circuit 1**

$$4.8\text{v} + 2.25\text{v} = 7.05 \text{ v}$$

### **Circuit 2**

$$1.3\text{v} + 5.6\text{v} = 6.9\text{v}$$

### **Circuit 3**

$$2.05\text{v} + 4.8\text{v} = 6.85\text{v}$$

### **Circuit 4**

$$3\text{v} + 3.9\text{v} = 6.9\text{v}$$

Also for each circuit the current leaving was approximately equal to the current entering the circuit, this proves Kirchhoff's Current Law.

### **Circuit 1**

$$10\text{mA} = 10\text{mA}$$

### **Circuit 2**

$$26\text{mA} = 25\text{mA} + 0\text{mA}$$

### **Circuit 3**

$$22\text{mA} = 21\text{mA} + 1\text{mA}$$

$$22\text{mA} = 22\text{mA}$$

### **Circuit 4**

$$13.5\text{mA} + 4.5\text{mA} = 18\text{mA}$$

$$18\text{mA} = 18\text{mA}$$

The resistance of the LED varies depending on how much voltage is going through it therefore we cannot use the multimeter to measure the resistance.

Kirchhoff's Law can be proven by assembling together a circuit with more than one resistor and it holds true in all cases.

## **REFERENCES**

- <http://physics.mercer.edu/labs/manuals/manualEMlab/Kirchhoff.pdf>
- [http://www.academia.edu/8750464/Electrical\\_Circuits\\_I\\_Experiment\\_2\\_-\\_Kirch\\_hoffs\\_Law](http://www.academia.edu/8750464/Electrical_Circuits_I_Experiment_2_-_Kirch_hoffs_Law)
- <https://www.khanacademy.org/science/electrical-engineering/ee-circuit-analysis-topic/ee-dc-circuit-analysis/a/ee-kirchhoffs-laws>
- <http://www.slideshare.net/khaileselassie/lab-1-kirchhoffs-voltage-and-current-laws-by-kehali-bekele-haileselassie>
- **Grob's Basic Electronics 11th Revised edition Edition**